



### \* Electrical Resistance is the opposition of the movement of electrons as they flow through a circuit

\* Measured in Ohms A

Wednesday, April 16, 2014

### Factors that Affect Resistance

- \* Factors that affect resistance
  - \* i) Type of material: if the material is a good conductor, resistance is low as electrons can travel easily
  - \* ii) Cross-Sectional area: The greater the cross sectionals area, the lower the resistance

## Factors that Affect Resistance

- \* Factors that affect resistance
  - \* iii)Length: The longer the wire the higher the resistance value
  - \* iv) Temperature: The cooler the substance, the lower the resistance
    - \* As a substance warms, the particles vibrate faster and there is more things for the electrons to run into

## Measuring Resistance

- \* Resistance is measured using an ohmmeter
- \* The ohmmeter is connected in parallel with the load
- \* Ohmmeters are represented by the following symbol

## Ohn's Law

### \* Current (I) is measured in amperes (A)

- \* Voltage (V) is measured in volts

\* Resistance (R) is measured in ohms (N)

\* Ohm's law states that as the potential difference across a load increases, so does the current

### Sample Calculation

# \* A 110 Λ resistor is connected to a power supply set at 1.2 V. Calculate the current going through the resistor.

## Sample Calculation







Wednesday, April 16, 2014

### Sample Calculation

### \* I = 1.2 V/ 110 A

### \* I = 0.01 A

## \* Therefore, the current through the resistor is 0.01 A.

Wednesday, April 16, 2014